

DPP


DAILY PRACTICE PROBLEMS

Class : XIIth
Date :





Subject : PHYSICS
DPP No. :4

Topic :-Alternating Current


- If coefficient of self induction of a coil is 1 H, an emf of 1 V is induced, if
 - Current flowing is 1 A
 - Current variation rate is 1 As^{-1}
 - Current of 1 A flows for one sec
 - None of the above
- A parallel plate capacitor C with plates of unit area and separation d is filled with a liquid of dielectric constant $K=2$. The level of liquid is $\frac{d}{3}$ initially. Suppose the liquid level decreases at a constant speed v , the time constant as a function of time t is.

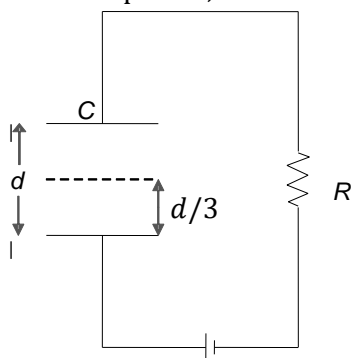

- $\frac{6\epsilon_0 R}{5d + 3vt}$
 - $\frac{(15d + 9vt)\epsilon_0 R}{2d^2 - 3dvt - 9v^2 t^2}$
 - $\frac{6\epsilon_0 R}{5d - 3vt}$
 - $\frac{(15d - 9vt)\epsilon_0 R}{2d^2 + 3dvt - 9v^2 t^2}$
- If the coils of a transformer are made up of thick wire, then
 - Eddy currents loss will be more
 - Magnetic flux leakage is reduced
 - Joule's heating loss is increased
 - Joule's heating loss is reduced
 - The peak value of 220 volts of ac mains is
 - 155.6 volts
 - 220.0 volts
 - 311.0 volts
 - 440 volts
 - An alternating emf is applied across a parallel combination of a resistance R , capacitance C and an inductance L . If I_R, I_L, I_C are the current through R, L and C respectively, then the diagram which correctly represents the phase relationship among I_R, I_L, I_C and source emf E , is given by

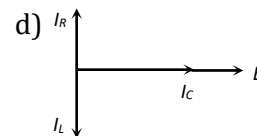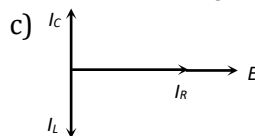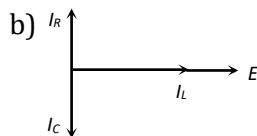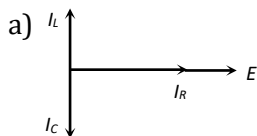

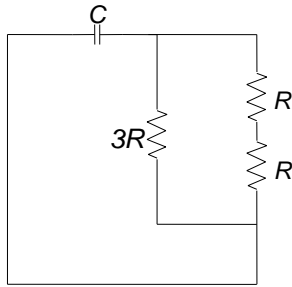6. The time constant of the given circuit is



- a) $\frac{3RC}{5}$ b) $\frac{6RC}{5}$ c) $\frac{5RC}{6}$ d) None of these

7. A solenoid has 2000 turns wound over a length of 0.30 m. The area of its cross section is $1.2 \times 10^{-3} \text{ m}^2$. Around its central section, a coil of 300 turns is wound. If an initial current of 2 A in the solenoid is reversed in 0.25 s, then the emf induced in the coil is equal to

- a) $6 \times 10^{-4} \text{ V}$ b) $4.8 \times 10^{-2} \text{ V}$ c) $6 \times 10^{-2} \text{ V}$ d) 48 kV

8. The potential difference V and the current i flowing through an instrument in an ac circuit of frequency f are given by $V = 5 \cos \omega t$ volts and $I = 2 \sin \omega t$ amperes (where $\omega = 2\pi f$). The power dissipated in the instrument is

- a) Zero b) 10 W c) 5 W d) 2.5 W

9. An e.m.f. $E = 4 \cos(1000t)$ volt is applied to an LR-circuit of inductance 3 mH and resistance 4 ohms. The amplitude of current in the circuit is

- a) $\frac{4}{\sqrt{7}} \text{ A}$ b) 1.0 A c) $\frac{4}{7} \text{ A}$ d) 0.8 A

10. A coil of inductive reactance 31Ω has a resistance of 8Ω . It is placed in series with a condenser of capacitive reactance 25Ω . The combination is connected to an a.c. source of 110 volt. The power factor of the circuit is

- a) 0.80 b) 0.33 c) 0.56 d) 0.64

11. The expression for magnetic induction inside a solenoid of length L , carrying a current i and having N number of turns is

- a) $\frac{\mu_0 N}{4\pi L} i$ b) $\mu_0 NLi$ c) $\frac{\mu_0}{4\pi} NLi$ d) $\mu_0 \frac{N^2}{L} i$

12. In an LR-circuit, the inductive reactance is equal to the resistance R of the circuit. An e.m.f. $E = E_0 \cos(\omega t)$ is applied to the circuit. The power consumed in the circuit is

- a) $\frac{E_0^2}{R}$ b) $\frac{E_0^2}{2R}$ c) $\frac{E_0^2}{4R}$ d) $\frac{E_0^2}{8R}$

13. In an AC circuit, the current lags behind the voltage by $\pi/3$. The components of the circuit are

- a) R and L b) L and C c) R and C d) Only R


14. The instantaneous value of current in an A.C. circuit is $I = 2 \sin(100\pi t + \pi/3)$ A. The current will be maximum for the first time at

- a) $t = \frac{1}{100} \text{ s}$ b) $t = \frac{1}{200} \text{ s}$ c) $t = \frac{1}{400} \text{ s}$ d) $t = \frac{1}{600} \text{ s}$

15. A resistor R , an inductor L and a capacitor C are connected in series to an oscillator of frequency n , if the resonant frequency is n_r , then the current lags behind voltage, when

- a) $n = 0$ b) $n < n_r$ c) $n = n_r$ d) $n > n_r$

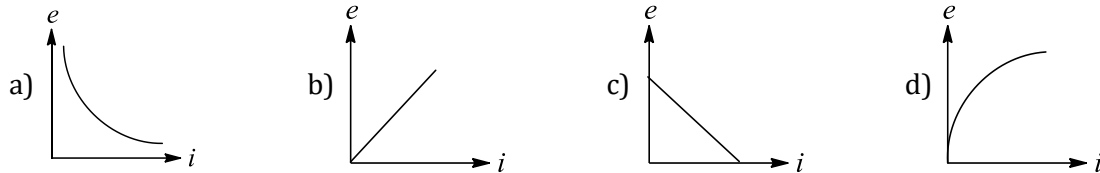16. During a current change from 2 A to 4 A in 0.05 s, 8 V of emf is developed in a coil. The coefficient of self-induction is
 a) 0.1 H b) 0.2 H c) 0.4 H d) 0.8 H
17. In an $L - R$ circuit shown in above figure switch S is closed at time $t = 0$. If e denotes the induced emf across inductor and i , the current in the circuit at any time t , then which of the following graphs, figure shows the variation of e with i ?



18. Let C be the capacitance of a capacitor discharging through a resistor R . Suppose t_1 is the time taken for the energy stored in the capacitor to reduce to half its initial value and t_2 is the time taken for the charge to reduce to one-fourth its initial value. Then the ratio $\frac{t_1}{t_2}$ will be
 a) 1 b) $\frac{1}{2}$ c) $\frac{1}{4}$ d) 2
19. The phase difference between the current and voltage of LCR circuit in series combination at resonance is
 a) 0 b) $\pi/2$ c) π d) $-\pi$
20. The impedance of a circuit consists of 3 ohm resistance and 4 ohm reactance. The power factor of the circuit is
 a) 0.4 b) 0.6 c) 0.8 d) 1.0